

We have obtained the following solutions for the **steady-state voltage** and **current phasors** in a transmission line:

### Loss-less line

$$V(z) = V^+ e^{-j\beta z} + V^- e^{j\beta z}$$

$$I(z) = \frac{1}{Z_0} \left( V^+ e^{-j\beta z} - V^- e^{j\beta z} \right)$$

### Lossy line


$$V(z) = V^+ e^{-\gamma z} + V^- e^{\gamma z}$$

$$I(z) = \frac{1}{Z_0} \left( V^+ e^{-\gamma z} - V^- e^{\gamma z} \right)$$

Since  $V(z)$  and  $I(z)$  are the solutions of **second order differential (wave) equations**, we must determine **two unknowns**,  $V^+$  and  $V^-$ , which represent the amplitudes of steady-state voltage waves, travelling in the **positive** and in the **negative** direction, respectively.

Therefore, we need **two boundary conditions** to determine these unknowns, by considering the effect of the **load** and of the **generator** connected to the transmission line.

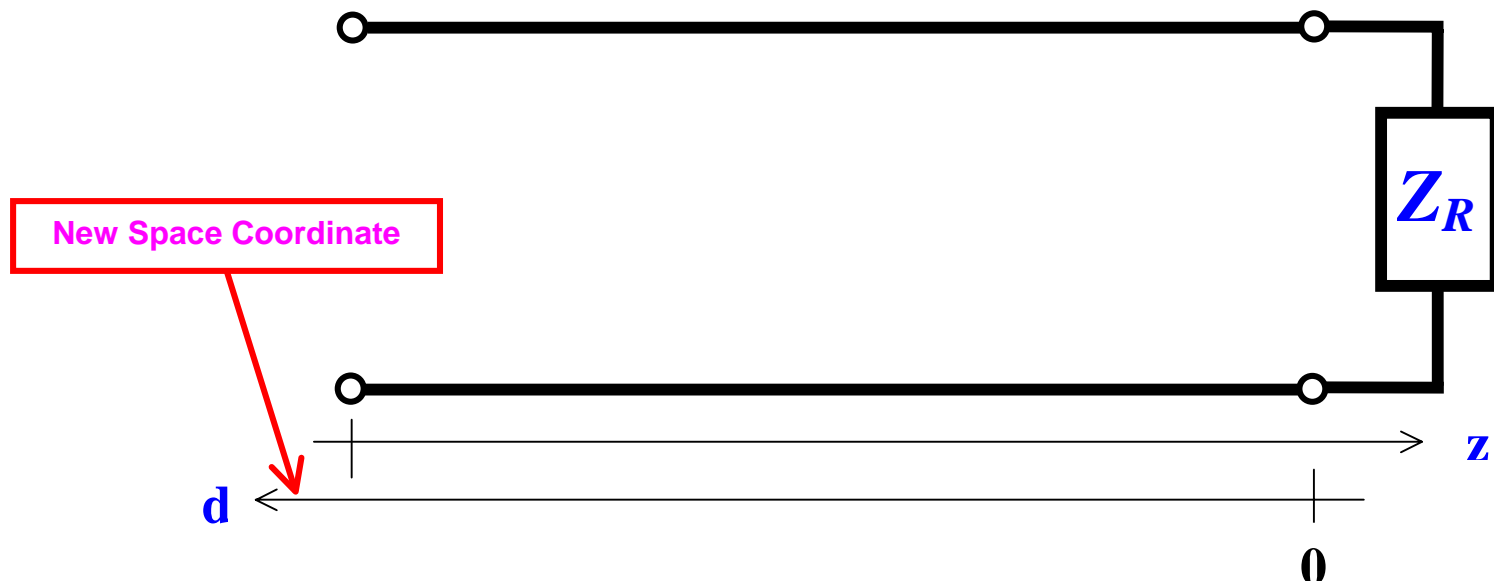Before we consider the boundary conditions, it is very convenient to shift the reference of the space coordinate so that the **zero reference is at the location of the load** instead of the generator. Since the analysis of the transmission line normally starts from the load itself, this will simplify considerably the problem later.



We will also change the **positive direction** of the space coordinate, so that it increases when moving **from load to generator** along the transmission line.

We adopt a new coordinate  $\mathbf{d} = -\mathbf{z}$ , with zero reference at the load location. The **new equations** for voltage and current along the lossy transmission line are

### Loss-less line

$$V(\mathbf{d}) = V^+ e^{j\beta \mathbf{d}} + V^- e^{-j\beta \mathbf{d}}$$

$$I(\mathbf{d}) = \frac{1}{Z_0} \left( V^+ e^{j\beta \mathbf{d}} - V^- e^{-j\beta \mathbf{d}} \right)$$

### Lossy line

$$V(\mathbf{d}) = V^+ e^{\gamma \mathbf{d}} + V^- e^{-\gamma \mathbf{d}}$$

$$I(\mathbf{d}) = \frac{1}{Z_0} \left( V^+ e^{\gamma \mathbf{d}} - V^- e^{-\gamma \mathbf{d}} \right)$$

At the **load** ( $\mathbf{d} = 0$ ) we have, for both cases,

$$V(0) = V^+ + V^-$$

$$I(0) = \frac{1}{Z_0} (V^+ - V^-)$$

For a given load impedance  $Z_R$ , the **load boundary condition** is

$$V(0) = Z_R I(0)$$

Therefore, we have

$$V^+ + V^- = \frac{Z_R}{Z_0} (V^+ - V^-)$$

from which we obtain the **voltage load reflection coefficient**

$$\Gamma_R = \frac{V^-}{V^+} = \frac{Z_R - Z_0}{Z_R + Z_0}$$

We can introduce this result into the transmission line equations as

**Loss-less line**

$$V(d) = V^+ e^{j\beta d} (1 + \Gamma_R e^{-2j\beta d})$$

$$I(d) = \frac{V^+ e^{j\beta d}}{Z_0} (1 - \Gamma_R e^{-2j\beta d})$$

**Lossy line**

$$V(d) = V^+ e^{\gamma d} (1 + \Gamma_R e^{-2\gamma d})$$

$$I(d) = \frac{V^+ e^{\gamma d}}{Z_0} (1 - \Gamma_R e^{-2\gamma d})$$

At each line location we define a **Generalized Reflection Coefficient**

$$\Gamma(d) = \Gamma_R e^{-2j\beta d}$$

$$\Gamma(d) = \Gamma_R e^{-2\gamma d}$$

and the line equations become

$$V(d) = V^+ e^{j\beta d} (1 + \Gamma(d))$$

$$I(d) = \frac{V^+ e^{j\beta d}}{Z_0} (1 - \Gamma(d))$$


$$V(d) = V^+ e^{\gamma d} (1 + \Gamma(d))$$

$$I(d) = \frac{V^+ e^{\gamma d}}{Z_0} (1 - \Gamma(d))$$

We define the **line impedance** as

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

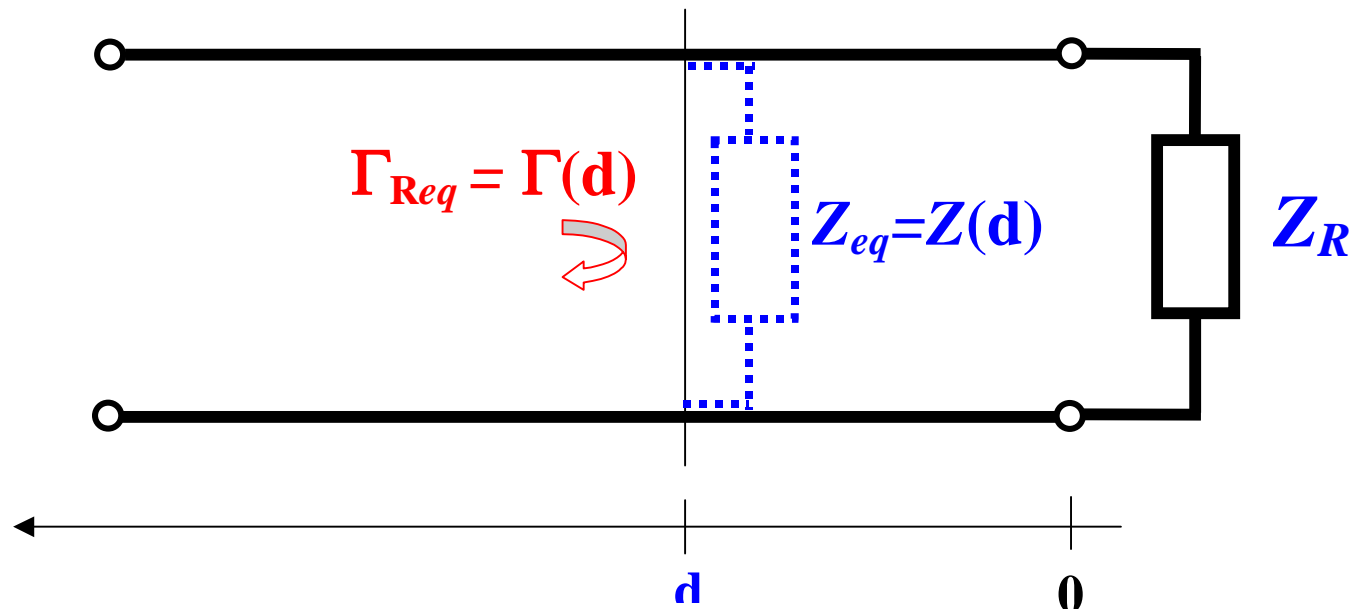A simple circuit diagram can illustrate the significance of line impedance and generalized reflection coefficient:



If you imagine to **cut** the line at location **d**, the input impedance of the portion of line terminated by the load is the same as the line impedance at that location “**before the cut**”. The behavior of the line on the **left** of location **d** is the same if an equivalent impedance with value **Z(d)** replaces the cut out portion. The reflection coefficient of the new load is equal to  **$\Gamma(d)$**

$$\Gamma_{Req} = \Gamma(d) = \frac{Z_{Req} - Z_0}{Z_{Req} + Z_0}$$

If the total length of the line is **L**, the input impedance is obtained from the formula for the line impedance as

$$Z_{in} = \frac{V_{in}}{I_{in}} = \frac{V(L)}{I(L)} = Z_0 \frac{1 + \Gamma(L)}{1 - \Gamma(L)}$$

The input impedance is the **equivalent impedance** representing the entire line terminated by the load.

An important practical case is the **low-loss transmission line**, where the **reactive elements** still dominate but  **$R$**  and  **$G$**  cannot be neglected as in a loss-less line. We have the following conditions:

$$\omega L \gg R \qquad \omega C \gg G$$

so that

$$\begin{aligned} \gamma &= \sqrt{(j\omega L + R)(j\omega C + G)} \\ &= \sqrt{j\omega L \ j\omega C \left(1 + \frac{R}{j\omega L}\right) \left(1 + \frac{G}{j\omega C}\right)} \\ &\approx j\omega\sqrt{LC} \sqrt{1 + \frac{R}{j\omega L} + \frac{G}{j\omega C} - \frac{RG}{\omega^2 LC}} \end{aligned}$$

The last term under the square root can be neglected, because it is the product of two very small quantities.

What remains of the square root can be **expanded** into a **truncated Taylor series**

$$\begin{aligned}\gamma &\approx j\omega\sqrt{LC}\left[1 + \frac{1}{2}\left(\frac{R}{j\omega L} + \frac{G}{j\omega C}\right)\right] \\ &= \frac{1}{2}\left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}}\right) + j\omega\sqrt{LC}\end{aligned}$$

so that

$$\alpha = \frac{1}{2}\left(R\sqrt{\frac{C}{L}} + G\sqrt{\frac{L}{C}}\right) \qquad \beta = \omega\sqrt{LC}$$

The **characteristic impedance** of the **low-loss line** is a **real** quantity for all practical purposes and it is approximately the same as in a corresponding **loss-less line**

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \approx \sqrt{\frac{L}{C}}$$

and the **phase velocity** associated to the wave propagation is

$$v_p = \frac{\omega}{\beta} \approx \frac{1}{\sqrt{LC}}$$

**BUT NOTE:**

**In the case of the low-loss line, the equations for voltage and current retain the same form obtained for general lossy lines.**

Again, we obtain the **loss-less transmission line** if we assume

$$R = 0$$

$$G = 0$$

This is often acceptable in relatively short transmission lines, where the overall attenuation is small.

As shown earlier, the characteristic impedance in a loss-less line is exactly real

$$Z_0 = \sqrt{\frac{L}{C}}$$

while the propagation constant has no attenuation term

$$\gamma = \sqrt{(j\omega L)(j\omega C)} = j\omega \sqrt{LC} = j\beta$$

**The loss-less line does not dissipate power**, because  $\alpha = 0$ .

For all cases, the line impedance was defined as

$$Z(d) = \frac{V(d)}{I(d)} = Z_0 \frac{1 + \Gamma(d)}{1 - \Gamma(d)}$$

By including the appropriate generalized reflection coefficient, we can derive alternative expressions of the line impedance:

**A) Loss-less line**

$$Z(d) = Z_0 \frac{1 + \Gamma_R e^{-2j\beta d}}{1 - \Gamma_R e^{-2j\beta d}} = Z_0 \frac{Z_R + jZ_0 \tan(\beta d)}{jZ_R \tan(\beta d) + Z_0}$$

**B) Lossy line (including low-loss)**

$$Z(d) = Z_0 \frac{1 + \Gamma_R e^{-2\gamma d}}{1 - \Gamma_R e^{-2\gamma d}} = Z_0 \frac{Z_R + Z_0 \tanh(\gamma d)}{Z_R \tanh(\gamma d) + Z_0}$$

Let's now consider **power flow in a transmission line**, limiting the discussion to the **time-average power**, which accounts for the **active power** dissipated by the **resistive** elements in the circuit.


**The time-average power at any transmission line location is**

$$\langle P(d, t) \rangle = \frac{1}{2} \operatorname{Re} \left\{ V(d) I^*(d) \right\}$$

This quantity indicates the time-average power that **flows** through the line cross-section at location **d**. In other words, this is the power that, given a certain input, is **able to reach** location **d** and then **flows** into the remaining portion of the line **beyond this point**.

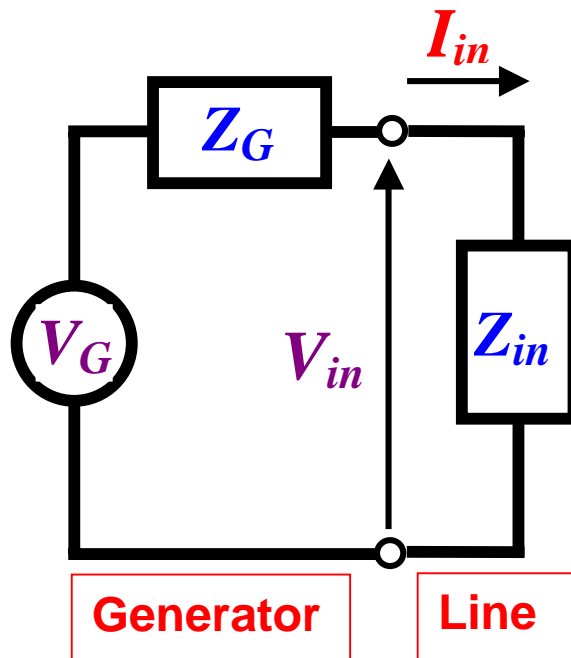**It is a common mistake to think that the quantity above is the power dissipated at location **d** !**

The **generator**, the **input impedance**, the **input voltage** and the **input current** determine the **power** injected at the transmission line input.



$$V_{in} = V_G \frac{Z_{in}}{Z_G + Z_{in}}$$

$$I_{in} = V_G \frac{1}{Z_G + Z_{in}}$$

$$\langle P_{in} \rangle = \frac{1}{2} \text{Re} \{ V_{in} I_{in}^* \}$$

The time-average power reaching the load of the transmission line is given by

$$\begin{aligned}\langle P(d=0, t) \rangle &= \frac{1}{2} \operatorname{Re} \left\{ V(0) I^*(0) \right\} \\ &= \frac{1}{2} \operatorname{Re} \left\{ V^+ (1 + \Gamma_R) \frac{1}{Z_0^*} \left( V^+ (1 - \Gamma_R) \right)^* \right\}\end{aligned}$$


This represents the **power dissipated by the load**.

The time-average power **absorbed by the line** is simply the difference between the input power and the power absorbed by the load

$$\langle P_{line} \rangle = \langle P_{in} \rangle - \langle P(d=0, t) \rangle$$

Remember that the internal impedance of the generator dissipates part of the total power generated.

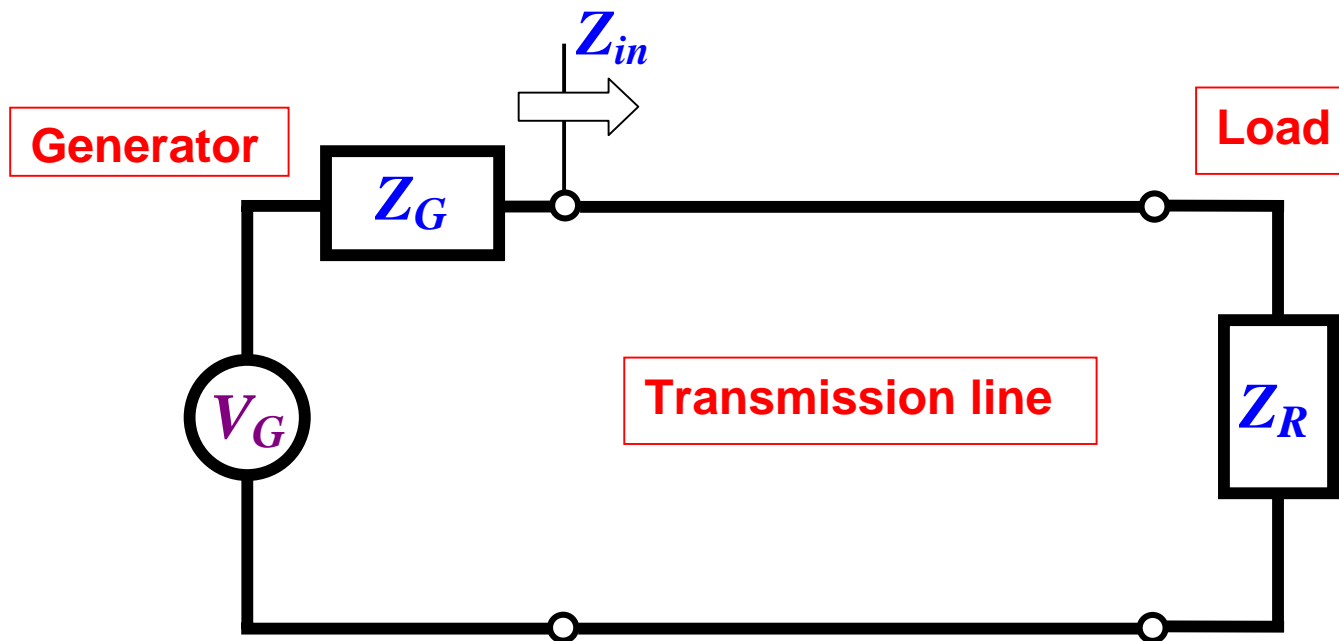The time-average power injected into the input of the transmission line is maximized when the input impedance of the transmission line and the internal generator impedance are complex conjugate of each other.



$$Z_G = Z_{in}^* \text{ for maximum power transfer}$$

In a **loss-less transmission line** no power is absorbed by the line, so the input time-average power is the same as the time-average power absorbed by the load. The characteristic impedance of the loss-less line is **real** and we can express the power flow as

$$\begin{aligned}
 \langle P(d, t) \rangle &= \frac{1}{2} \operatorname{Re} \left\{ V(d) I^*(d) \right\} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V^+ e^{j\beta d} \left( 1 + \Gamma_R e^{-j2\beta d} \right) \right. \\
 &\quad \left. \frac{1}{Z_0} (V^+)^* e^{-j\beta d} \left( 1 - \Gamma_R e^{-j2\beta d} \right)^* \right\} \\
 &= \underbrace{\frac{1}{2Z_0} |V^+|^2}_{\text{Incident wave}} - \underbrace{\frac{1}{2Z_0} |V^+|^2 |\Gamma_R|^2}_{\text{Reflected wave}}
 \end{aligned}$$

In the case of **low-loss** lines, the **characteristic impedance** is again **real**, and the time-average power flow along the line is given by

$$\begin{aligned}
 \langle P(d, t) \rangle &= \frac{1}{2} \operatorname{Re} \left\{ V(d) I^*(d) \right\} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V^+ e^{\alpha d} e^{j\beta d} \left( 1 + \Gamma_R e^{-2\gamma d} \right) \right. \\
 &\quad \left. \frac{1}{Z_0} (V^+)^* e^{\alpha d} e^{-j\beta d} \left( 1 - \Gamma_R e^{-2\gamma d} \right)^* \right\} \\
 &= \underbrace{\frac{1}{2Z_0} |V^+|^2 e^{2\alpha d}}_{\text{Incident wave}} - \underbrace{\frac{1}{2Z_0} |V^+|^2 e^{-2\alpha d} |\Gamma_R|^2}_{\text{Reflected wave}}
 \end{aligned}$$

Note that in a **lossy line** the **reference** for the amplitude of the **incident voltage wave** is at the load and that the amplitude grows exponentially moving towards the input. The amplitude of the incident wave behaves in the following way

$$\underbrace{V^+ e^{\alpha L}}_{\text{input}} \Leftrightarrow \underbrace{V^+ e^{\alpha d}}_{\text{inside the line}} \Leftrightarrow \underbrace{V^+}_{\text{load}}$$

The **reflected voltage wave** has maximum amplitude at the load, and it decays exponentially moving back towards the generator. The amplitude of the reflected wave behaves in the following way

$$\underbrace{V^+ \Gamma_R e^{-\alpha L}}_{\text{input}} \Leftrightarrow \underbrace{V^+ \Gamma_R e^{-\alpha d}}_{\text{inside the line}} \Leftrightarrow \underbrace{V^+ \Gamma_R}_{\text{load}}$$

For a general **lossy line** the **characteristic impedance is complex**, and the time-average power is

$$\begin{aligned}
 \langle P(d, t) \rangle &= \frac{1}{2} \operatorname{Re} \left\{ V(d) I^*(d) \right\} \\
 &= \frac{1}{2} \operatorname{Re} \left\{ V^+ e^{\alpha d} e^{j\beta d} (1 + \Gamma(d)) \right. \\
 &\quad \left. Y_0^* (V^+)^* e^{\alpha d} e^{-j\beta d} (1 - \Gamma(d))^* \right\} \\
 &= \frac{G_0}{2} |V^+|^2 e^{2\alpha d} - \frac{G_0}{2} |V^+|^2 e^{-2\alpha d} |\Gamma_R|^2 \\
 &\quad + B_0 |V^+|^2 e^{2\alpha d} \operatorname{Im}(\Gamma(d))
 \end{aligned}$$

We have introduced for convenience the **characteristic admittance** of the line

$$Y_0 = \frac{1}{Z_0} = G_0 + jB_0$$

since a complex characteristic impedance would appear at denominator in the expression for the power.

Note that for a **low-loss** transmission line the characteristic impedance is approximately real and

$$B_0 \approx 0$$

The previous result for the low-loss line can be readily recovered from the time-average power for the general lossy line.

To completely specify the transmission line problem, we still have to determine the value of  $V_+$  from the **input boundary condition**.

- The **load boundary condition** imposes the shape of the interference pattern of voltage and current along the line.
- The **input boundary condition**, linked to the generator, imposes the scaling for the interference patterns.

We have

$$V_{in} = V(L) = V_G \frac{Z_{in}}{Z_G + Z_{in}} \quad \text{with} \quad Z_{in} = Z_0 \frac{1 + \Gamma(L)}{1 - \Gamma(L)}$$

$$\text{or} \quad \begin{cases} Z_{in} = Z_0 \frac{Z_R + jZ_0 \tan(\beta L)}{jZ_R \tan(\beta L) + Z_0} & \text{loss - less line} \\ Z_{in} = Z_0 \frac{Z_R + Z_0 \tanh(\gamma L)}{Z_R \tanh(\gamma L) + Z_0} & \text{lossy line} \end{cases}$$

For a **loss-less** transmission line:

$$V(L) = V^+ e^{j\beta L} [1 + \Gamma(L)] = V^+ e^{j\beta L} (1 + \Gamma_R e^{-j2\beta L})$$

$$\Rightarrow V^+ = V_G \frac{Z_{in}}{Z_G + Z_{in}} \frac{1}{e^{j\beta L} (1 + \Gamma_R e^{-j2\beta L})}$$


For a **lossy** transmission line:

$$V(L) = V^+ e^{\gamma L} [1 + \Gamma(L)] = V^+ e^{\gamma L} (1 + \Gamma_R e^{-2\gamma L})$$

$$\Rightarrow V^+ = V_G \frac{Z_{in}}{Z_G + Z_{in}} \frac{1}{e^{\gamma L} (1 + \Gamma_R e^{-2\gamma L})}$$


In order to have good **control** on the behavior of a high frequency circuit, it is very important to realize transmission lines as **uniform** as possible along their length, so that the impedance behavior of the line does not vary and can be easily characterized.

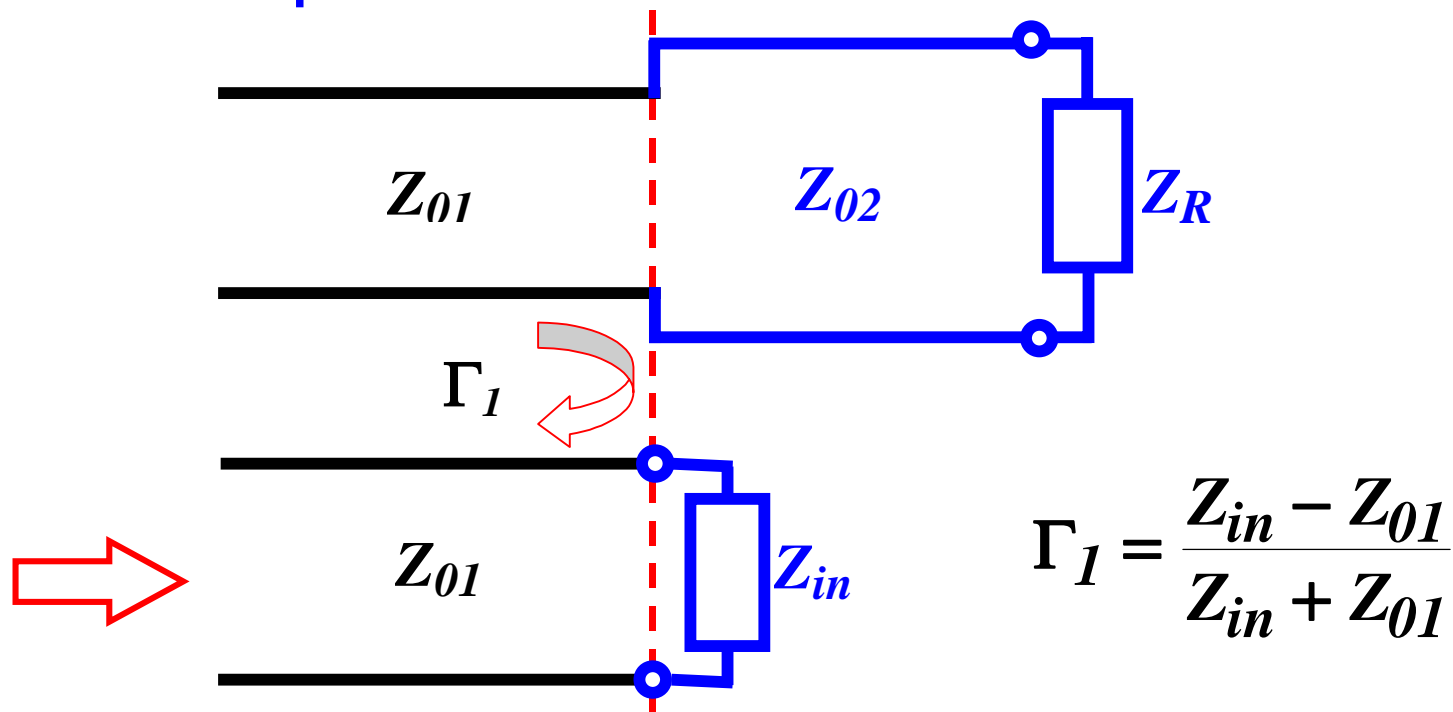A change in transmission line properties, wanted or unwanted, entails a change in the characteristic impedance, which causes a reflection. Example:



## Special Cases

$Z_R \rightarrow 0$  (SHORT CIRCUIT)

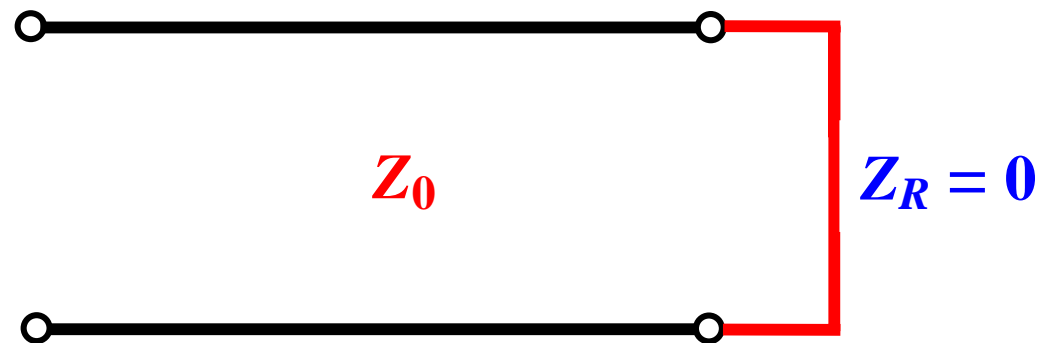

The load **boundary condition** due to the short circuit is  $V(0) = 0$

$$\Rightarrow V(d=0) = V^+ e^{j\beta 0} (1 + \Gamma_R e^{-j2\beta 0})$$

$$= V^+ (1 + \Gamma_R) = 0$$

$$\Rightarrow \Gamma_R = -1$$

Since

$$\Gamma_R = \frac{V^-}{V^+}$$
$$\Rightarrow V^- = -V^+$$

We can write the **line voltage** phasor as

$$\begin{aligned} V(d) &= V^+ e^{j\beta d} + V^- e^{-j\beta d} \\ &= V^+ e^{j\beta d} - V^+ e^{-j\beta d} \\ &= V^+ (e^{j\beta d} - e^{-j\beta d}) \\ &= 2jV^+ \sin(\beta d) \end{aligned}$$

For the **line current** phasor we have

$$\begin{aligned}
 I(d) &= \frac{1}{Z_0} (V^+ e^{j\beta d} - V^- e^{-j\beta d}) \\
 &= \frac{1}{Z_0} (V^+ e^{j\beta d} + V^+ e^{-j\beta d}) \\
 &= \frac{V^+}{Z_0} (e^{j\beta d} + e^{-j\beta d}) \\
 &= \frac{2V^+}{Z_0} \cos(\beta d)
 \end{aligned}$$

The **line impedance** is given by

$$Z(d) = \frac{V(d)}{I(d)} = \frac{2jV^+ \sin(\beta d)}{2V^+ \cos(\beta d) / Z_0} = jZ_0 \tan(\beta d)$$

The **time-dependent** values of voltage and current are obtained as

$$\begin{aligned}
 V(d, t) &= \text{Re}[V(d) e^{j\omega t}] = \text{Re}[2j |V^+| e^{j\theta} \sin(\beta d) e^{j\omega t}] \\
 &= 2 |V^+| \sin(\beta d) \cdot \text{Re}[j e^{j(\omega t + \theta)}] \\
 &= 2 |V^+| \sin(\beta d) \cdot \text{Re}[j \cos(\omega t + \theta) - \sin(\omega t + \theta)] \\
 &= -2 |V^+| \sin(\beta d) \sin(\omega t + \theta)
 \end{aligned}$$

$$\begin{aligned}
 I(d, t) &= \text{Re}[I(d) e^{j\omega t}] = \text{Re}[2 |V^+| e^{j\theta} \cos(\beta d) e^{j\omega t}] / Z_0 \\
 &= 2 |V^+| \cos(\beta d) \cdot \text{Re}[e^{j(\omega t + \theta)}] / Z_0 \\
 &= 2 |V^+| \cos(\beta d) \cdot \text{Re}[(\cos(\omega t + \theta) + j \sin(\omega t + \theta))] / Z_0 \\
 &= 2 \frac{|V^+|}{Z_0} \cos(\beta d) \cos(\omega t + \theta)
 \end{aligned}$$

The **time-dependent power** is given by

$$\begin{aligned}
 P(d, t) &= V(d, t) \cdot I(d, t) \\
 &= -4 \frac{|V^+|^2}{Z_0} \sin(\beta d) \cos(\beta d) \sin(\omega t + \theta) \cos(\omega t + \theta) \\
 &= -\frac{|V^+|^2}{Z_0} \sin(2\beta d) \sin(2\omega t + 2\theta)
 \end{aligned}$$

and the corresponding **time-average power** is

$$\begin{aligned}
 \langle P(d, t) \rangle &= \frac{1}{T} \int_0^T P(d, t) dt \\
 &= -\frac{|V^+|^2}{Z_0} \sin(2\beta d) \frac{1}{T} \int_0^T \sin(2\omega t + 2\theta) dt = 0
 \end{aligned}$$

$$Z_R \rightarrow \infty \text{ (OPEN CIRCUIT)}$$



$$Z_0$$

$$Z_R \rightarrow \infty$$



The load **boundary condition** due to the open circuit is  $I(0) = 0$

$$\Rightarrow I(d=0) = \frac{V^+}{Z_0} e^{j\beta 0} (1 - \Gamma_R e^{-j2\beta 0})$$

$$= \frac{V^+}{Z_0} (1 - \Gamma_R) = 0$$

$$\Rightarrow \Gamma_R = 1$$

Since

$$\Gamma_R = \frac{V^-}{V^+}$$
$$\Rightarrow V^- = V^+$$

We can write the **line current** phasor as

$$\begin{aligned} I(d) &= \frac{1}{Z_0} (V^+ e^{j\beta d} - V^- e^{-j\beta d}) \\ &= \frac{1}{Z_0} (V^+ e^{j\beta d} - V^+ e^{-j\beta d}) \\ &= \frac{V^+}{Z_0} (e^{j\beta d} - e^{-j\beta d}) = \frac{2jV^+}{Z_0} \sin(\beta d) \end{aligned}$$

For the **line voltage** phasor we have

$$\begin{aligned}
 V(d) &= (V^+ e^{j\beta d} + V^- e^{-j\beta d}) \\
 &= (V^+ e^{j\beta d} + V^+ e^{-j\beta d}) \\
 &= V^+ (e^{j\beta d} + e^{-j\beta d}) \\
 &= 2V^+ \cos(\beta d)
 \end{aligned}$$

The **line impedance** is given by

$$Z(d) = \frac{V(d)}{I(d)} = \frac{2V^+ \cos(\beta d)}{2jV^+ \sin(\beta d) / Z_0} = -j \frac{Z_0}{\tan(\beta d)}$$

The **time-dependent** values of voltage and current are obtained as

$$\begin{aligned}
 V(d, t) &= \text{Re}[V(d) e^{j\omega t}] = \text{Re}[2 |V^+| e^{j\theta} \cos(\beta d) e^{j\omega t}] \\
 &= 2 |V^+| \cos(\beta d) \cdot \text{Re}[e^{j(\omega t + \theta)}] \\
 &= 2 |V^+| \cos(\beta d) \cdot \text{Re}[(\cos(\omega t + \theta) + j \sin(\omega t + \theta))] \\
 &= 2 |V^+| \cos(\beta d) \cos(\omega t + \theta)
 \end{aligned}$$

$$\begin{aligned}
 I(d, t) &= \text{Re}[I(d) e^{j\omega t}] = \text{Re}[2j |V^+| e^{j\theta} \sin(\beta d) e^{j\omega t}] / Z_0 \\
 &= 2 |V^+| \sin(\beta d) \cdot \text{Re}[j e^{j(\omega t + \theta)}] / Z_0 \\
 &= 2 |V^+| \sin(\beta d) \cdot \text{Re}[j \cos(\omega t + \theta) - \sin(\omega t + \theta)] / Z_0 \\
 &= -2 \frac{|V^+|}{Z_0} \sin(\beta d) \sin(\omega t + \theta)
 \end{aligned}$$


The **time-dependent power** is given by

$$\begin{aligned}
 P(d, t) &= V(d, t) \cdot I(d, t) = \\
 &= -4 \frac{|V^+|^2}{Z_0} \cos(\beta d) \sin(\beta d) \cos(\omega t + \theta) \sin(\omega t + \theta) \\
 &= -\frac{|V^+|^2}{Z_0} \sin(2\beta d) \sin(2\omega t + 2\theta)
 \end{aligned}$$

and the corresponding **time-average power** is

$$\begin{aligned}
 \langle P(d, t) \rangle &= \frac{1}{T} \int_0^T P(d, t) dt \\
 &= -\frac{|V^+|^2}{Z_0} \sin(2\beta d) \frac{1}{T} \int_0^T \sin(2\omega t + 2\theta) dt = 0
 \end{aligned}$$

$$Z_R = Z_0 \text{ (MATCHED LOAD)}$$

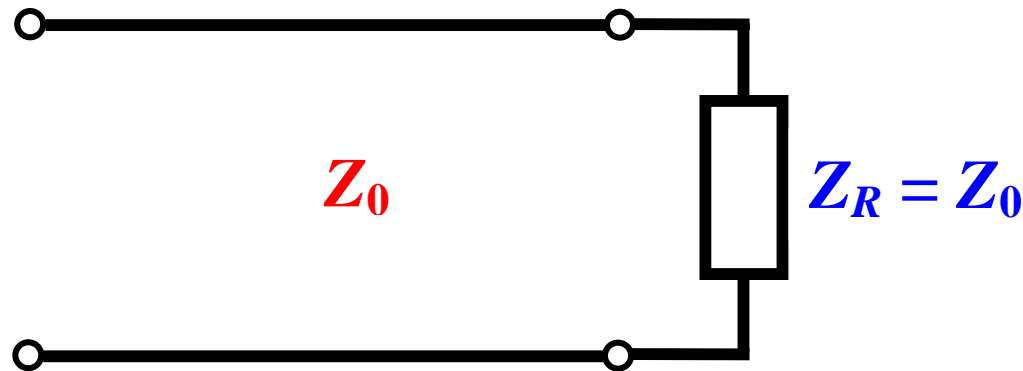

The **reflection coefficient** for a matched load is

$$\Gamma_R = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0 \quad \text{no reflection!}$$

The **line voltage** and **line current** phasors are

$$V(d) = V^+ e^{j\beta d} (1 + \Gamma_R e^{-2j\beta d}) = V^+ e^{j\beta d}$$

$$I(d) = \frac{V^+}{Z_0} e^{j\beta d} (1 - \Gamma_R e^{-2j\beta d}) = \frac{V^+}{Z_0} e^{j\beta d}$$

The **line impedance** is **independent** of position and equal to the characteristic impedance of the line

$$Z(d) = \frac{V(d)}{I(d)} = \frac{V^+ e^{j\beta d}}{\frac{V^+}{Z_0} e^{j\beta d}} = Z_0$$

The **time-dependent** voltage and current are

$$\begin{aligned} V(d, t) &= \text{Re}[|V^+| e^{j\theta} e^{j\beta d} e^{j\omega t}] \\ &= |V^+| \cdot \text{Re}[e^{j(\omega t + \beta d + \theta)}] = |V^+| \cos(\omega t + \beta d + \theta) \end{aligned}$$

$$\begin{aligned} I(d, t) &= \text{Re}[|V^+| e^{j\theta} e^{j\beta d} e^{j\omega t}] / Z_0 \\ &= \frac{|V^+|}{Z_0} \cdot \text{Re}[e^{j(\omega t + \beta d + \theta)}] = \frac{|V^+|}{Z_0} \cos(\omega t + \beta d + \theta) \end{aligned}$$

The **time-dependent power** is

$$P(d, t) = |V^+| \cos(\omega t + \beta d + \theta) \frac{|V^+|}{Z_0} \cos(\omega t + \beta d + \theta)$$


$$= \frac{|V^+|^2}{Z_0} \cos^2(\omega t + \beta d + \theta)$$

and the **time average power** absorbed by the load is

$$\langle P(d) \rangle = \frac{1}{T} \int_0^T \frac{|V^+|^2}{Z_0} \cos^2(\omega t + \beta d + \theta) dt$$

$$= \frac{|V^+|^2}{2Z_0}$$

$$Z_R = jX \text{ (PURE REACTANCE)}$$

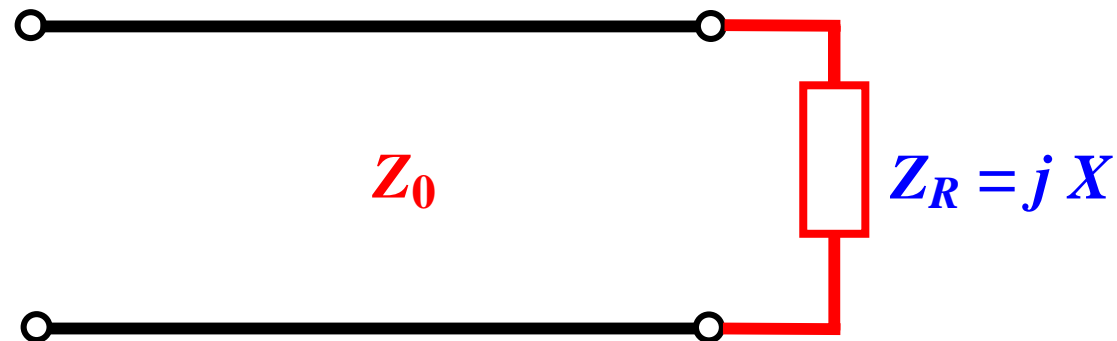

The **reflection coefficient** for a purely reactive load is

$$\begin{aligned} \Gamma_R &= \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{jX - Z_0}{jX + Z_0} = \\ &= \frac{(jX - Z_0)(jX - Z_0)}{(jX + Z_0)(jX - Z_0)} = \frac{X^2 - Z_0^2}{Z_0^2 + X^2} + 2j \frac{XZ_0}{Z_0^2 + X^2} \end{aligned}$$

In polar form

$$\Gamma_R = |\Gamma_R| \exp(j\theta)$$

where

$$|\Gamma_R| = \sqrt{\frac{(X^2 - Z_0^2)^2}{(Z_0^2 + X^2)^2} + \frac{4X^2 Z_0^2}{(Z_0^2 + X^2)^2}} = \sqrt{\frac{(Z_0^2 + X^2)^2}{(Z_0^2 + X^2)^2}} = 1$$

$$\theta = \tan^{-1} \left( \frac{2XZ_0}{X^2 - Z_0^2} \right)$$

The **reflection coefficient** has **unitary** magnitude, as in the case of short and open circuit load, with zero time average power absorbed by the load. Both voltage and current are finite at the load, and the time-dependent power oscillates between positive and negative values. This means that the load periodically stores and returns powers to the line without dissipation.

**Reactive impedances** can be realized with **transmission lines** terminated by a short or by an open circuit. The input impedance of a loss-less transmission line of length **L** terminated by a **short circuit** is purely imaginary


$$Z_{in} = j Z_0 \tan(\beta L) = j Z_0 \tan\left(\frac{2\pi}{\lambda} L\right) = j Z_0 \tan\left(\frac{2\pi f}{v_p} L\right)$$


At a specified frequency  $f$ , **any reactance value** can be obtained by changing the length of the line from 0 to  $\lambda/2$ . Since the tangent function is periodic, the behavior of the impedance will repeat identically for each line increment of length  $\lambda/2$ .

**Note that a similar periodic behavior is obtained when the length of the transmission line is fixed and the frequency of operation is changed.**

## Shorted transmission line – Fixed frequency

$L$ ↓	$L = 0$	$Z_{in} = 0$	short circuit	}
	$0 < L < \frac{\lambda}{4}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{\lambda}{4}$	$Z_{in} \rightarrow \infty$	open circuit	
	$\frac{\lambda}{4} < L < \frac{\lambda}{2}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{\lambda}{2}$	$Z_{in} = 0$	short circuit	}
	$\frac{\lambda}{2} < L < \frac{3\lambda}{4}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{3\lambda}{4}$	$Z_{in} \rightarrow \infty$	open circuit	
	$\frac{3\lambda}{4} < L < \lambda$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
...				

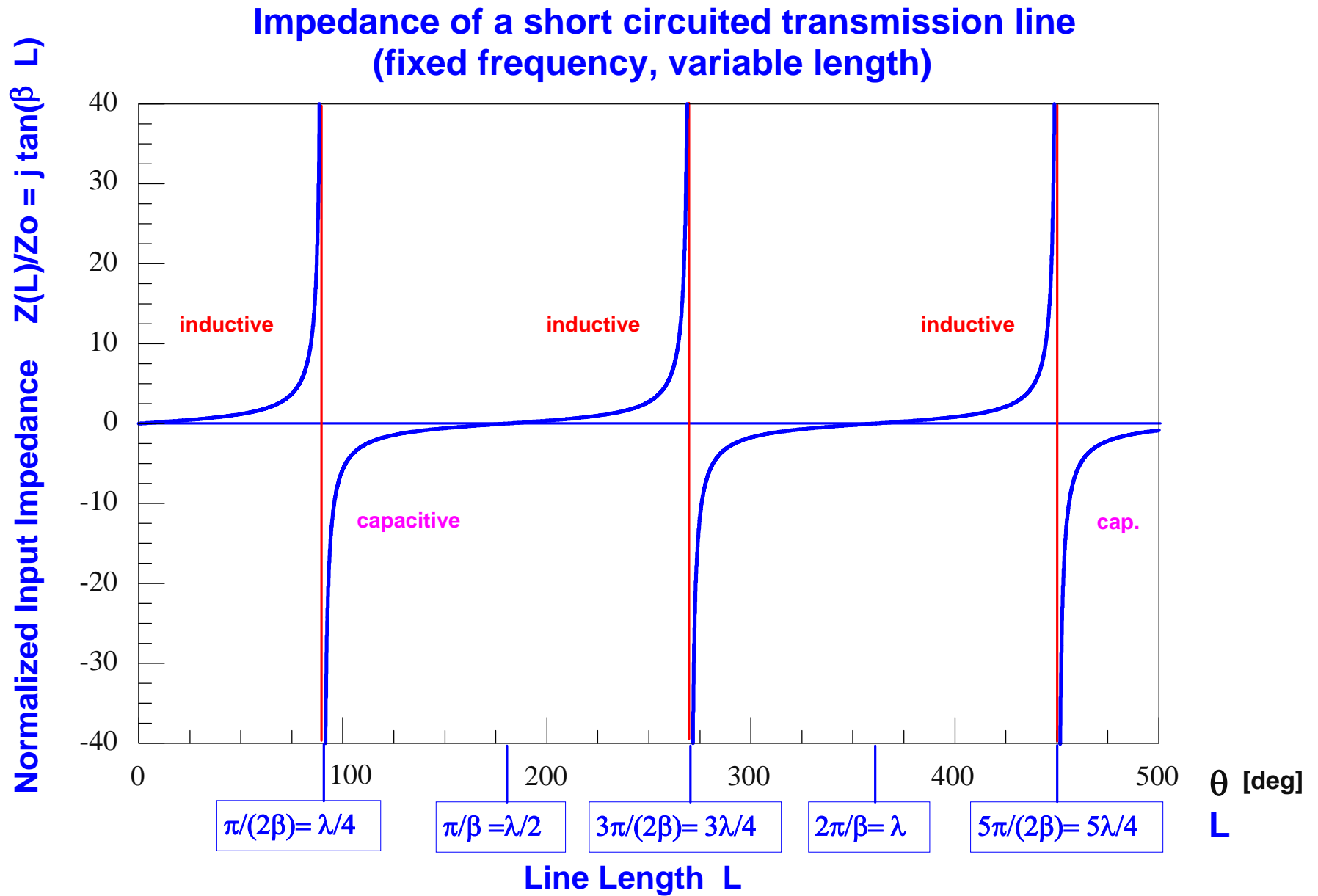

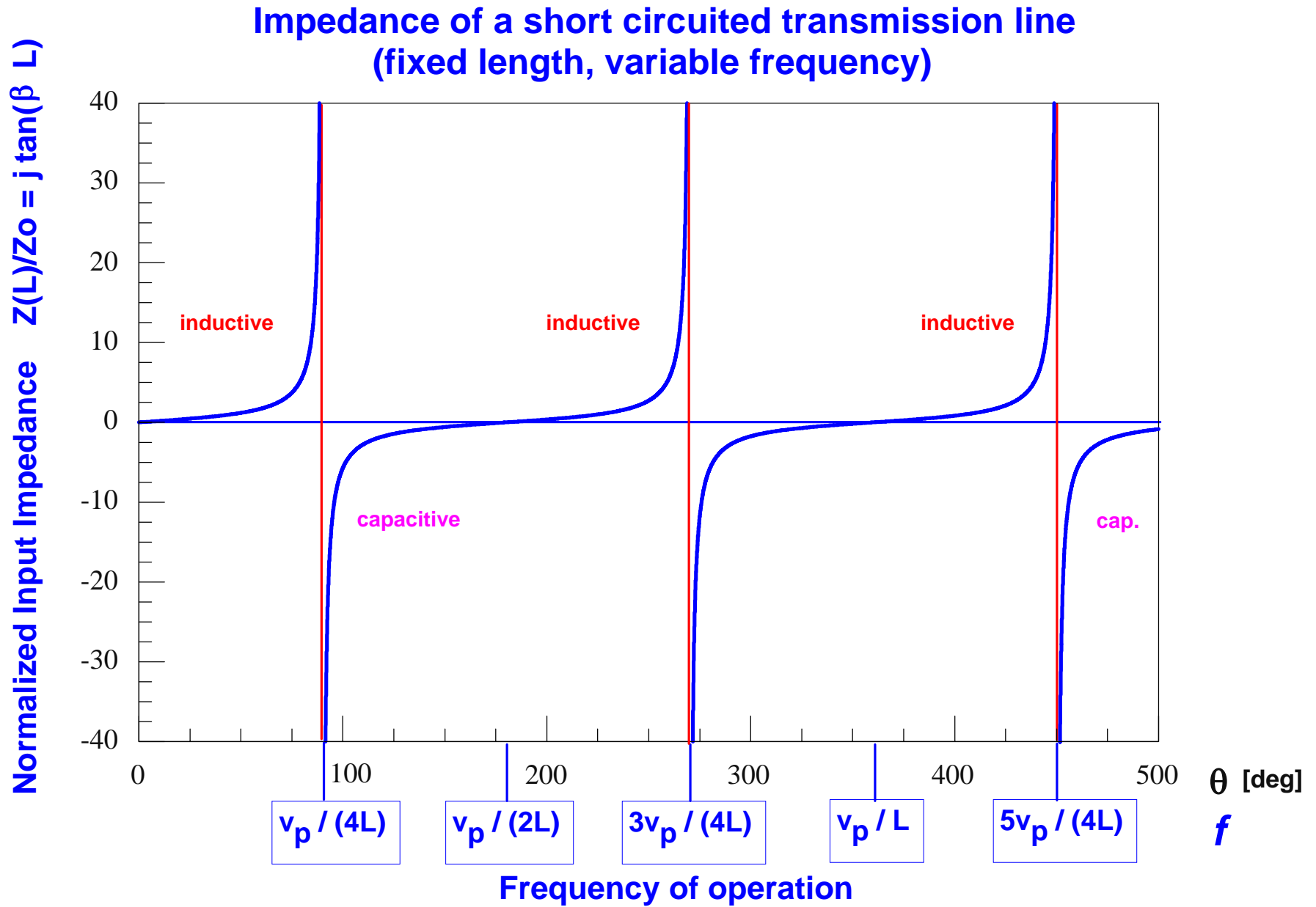

For a transmission line of length **L** terminated by an open circuit, the input impedance is again purely imaginary

$$Z_{in} = -j \frac{Z_0}{\tan(\beta L)} = -j \frac{Z_0}{\tan\left(\frac{2\pi}{\lambda} L\right)} = -j \frac{Z_0}{\tan\left(\frac{2\pi f}{v_p} L\right)}$$

We can use the open circuited line to realize any reactance, but starting from a **capacitive** value when the line length is very short.

The reactance varies **linearly** with frequency in the case of lumped elements since


$$X = \omega L \text{ (inductance)} \quad \text{or} \quad X = \frac{1}{\omega C} \text{ (capacitance)}$$

**This is not the case when the reactance is realized with a section of transmission line.**


## Open transmission line – Fixed frequency

$L$ ↓	$L = 0$	$Z_{in} \rightarrow \infty$	open circuit	}
	$0 < L < \frac{\lambda}{4}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{\lambda}{4}$	$Z_{in} = 0$	short circuit	
	$\frac{\lambda}{4} < L < \frac{\lambda}{2}$	$\text{Im}\{Z_{in}\} > 0$	inductance	
	$L = \frac{\lambda}{2}$	$Z_{in} \rightarrow \infty$	open circuit	}
	$\frac{\lambda}{2} < L < \frac{3\lambda}{4}$	$\text{Im}\{Z_{in}\} < 0$	capacitance	
	$L = \frac{3\lambda}{4}$	$Z_{in} = 0$	short circuit	
	$\frac{3\lambda}{4} < L < \lambda$	$\text{Im}\{Z_{in}\} > 0$	inductance	
...				

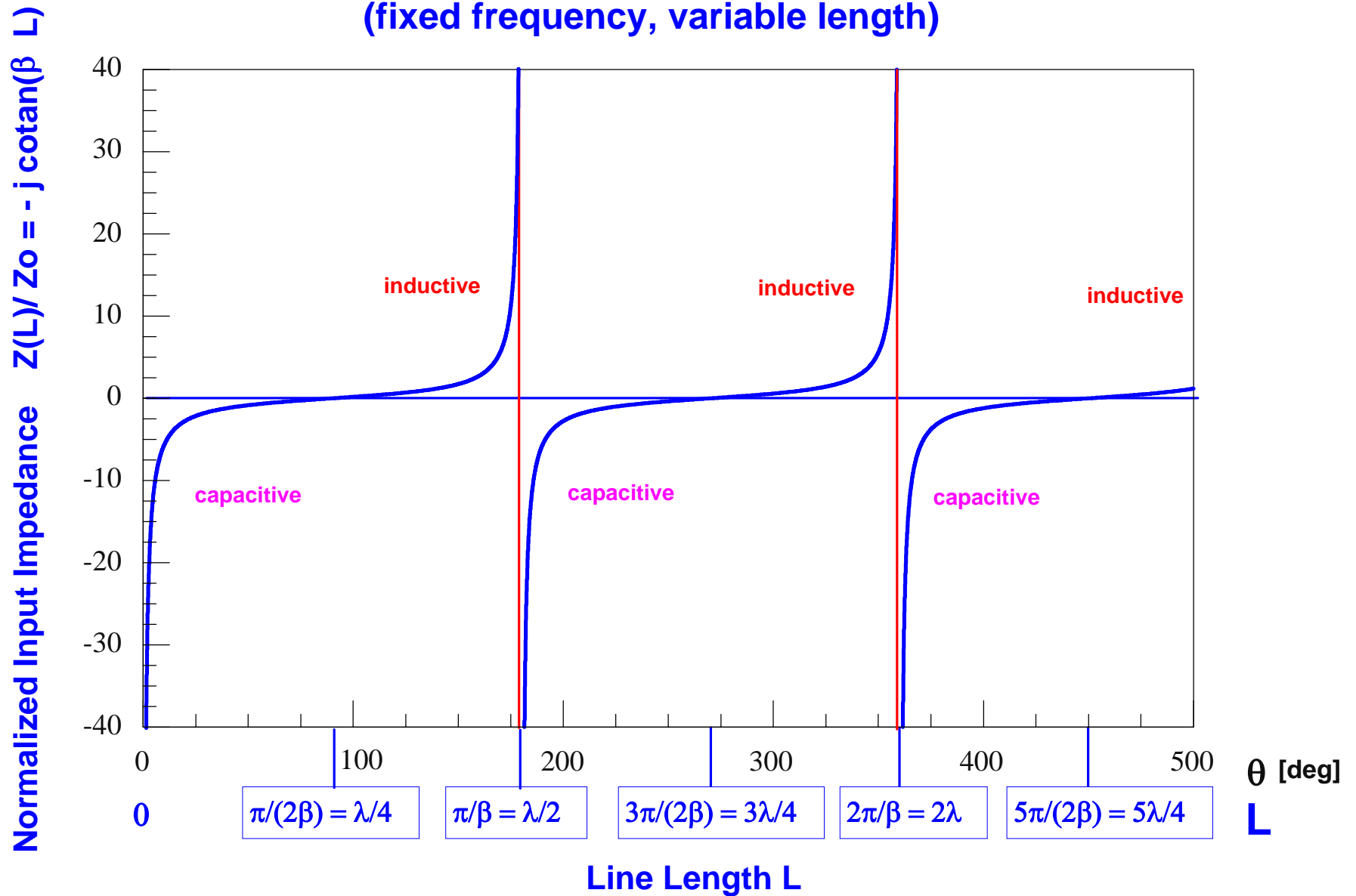
## Impedance of an open circuited transmission line (fixed frequency, variable length)


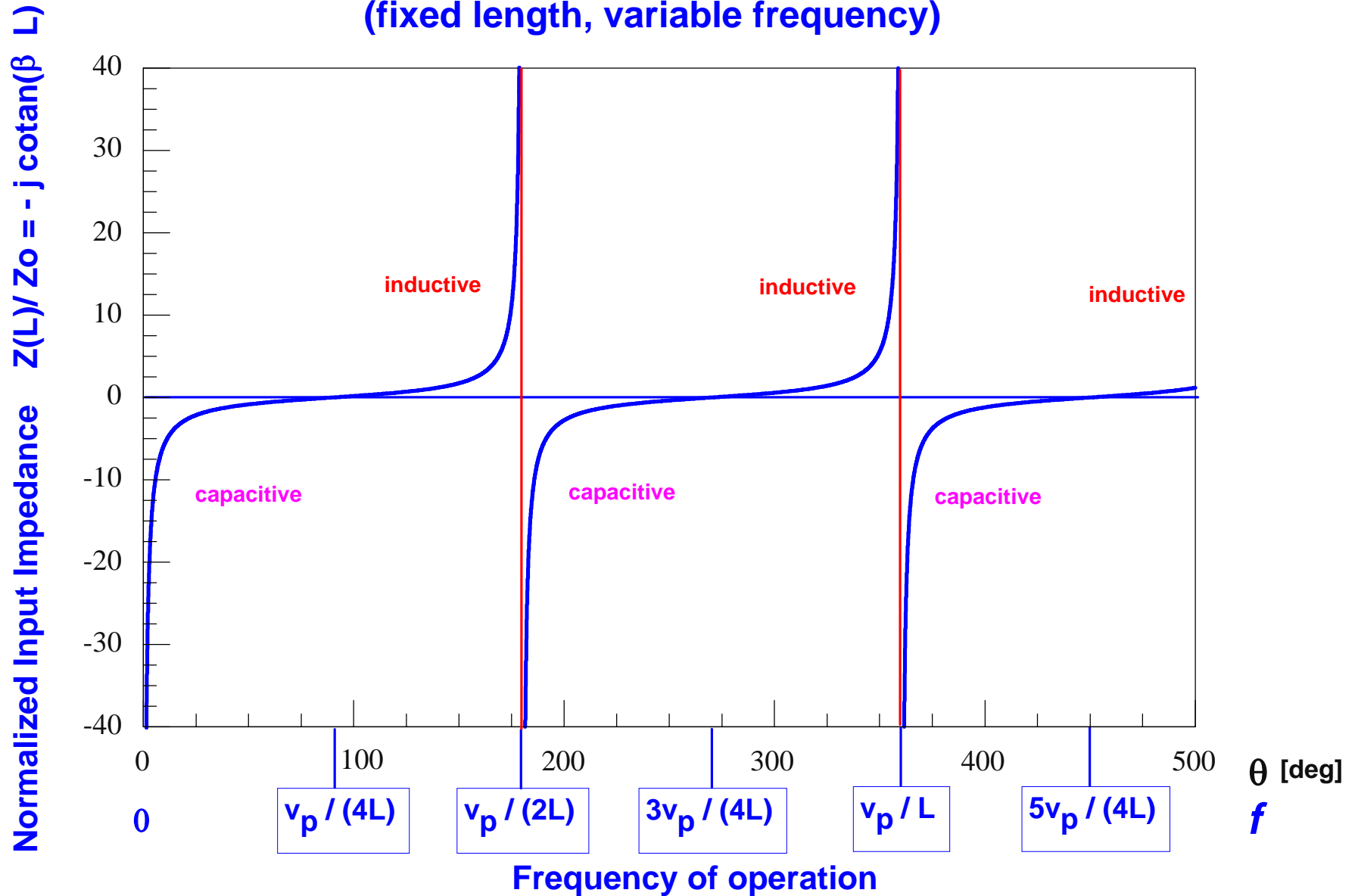
## Impedance of an open circuited transmission line (fixed length, variable frequency)



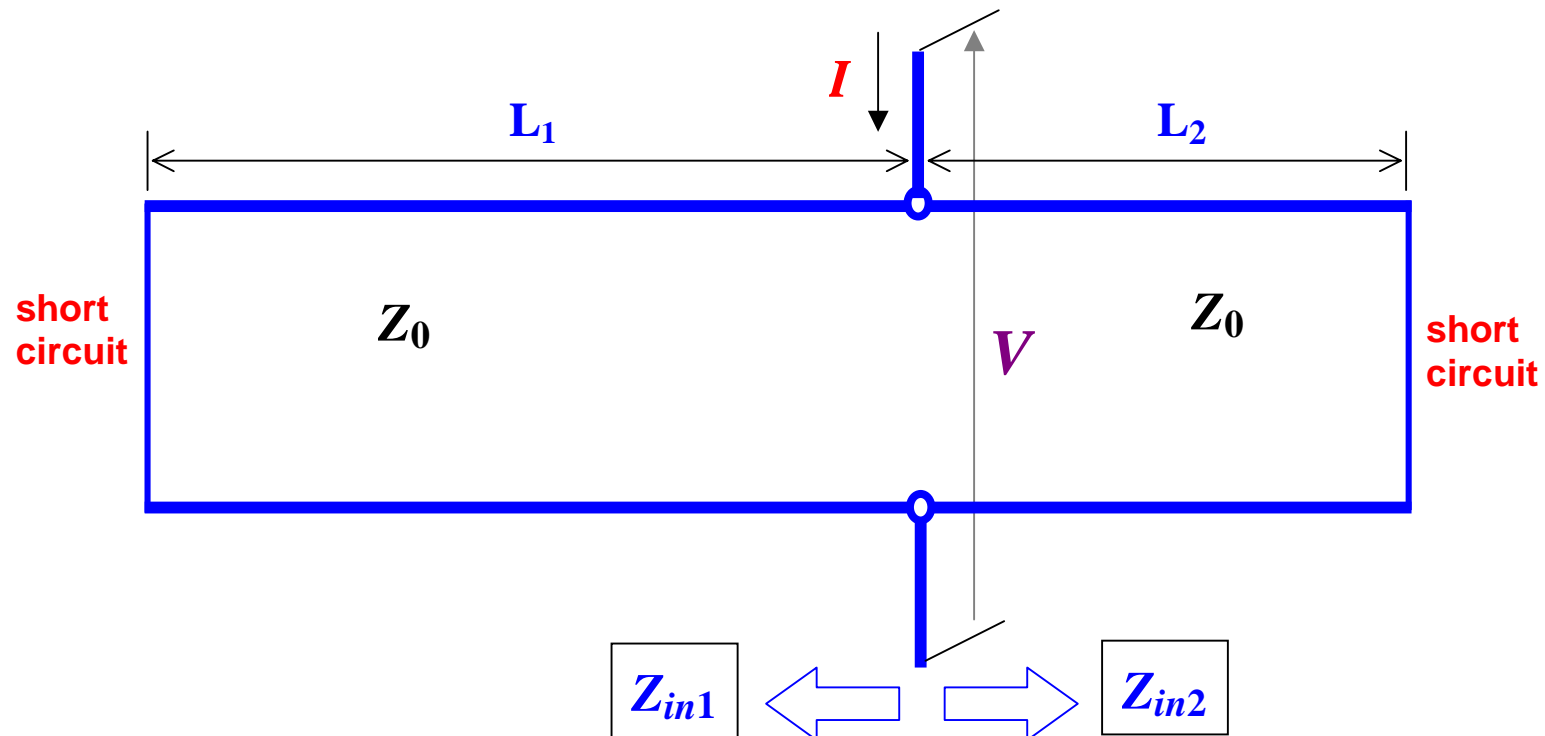It is possible to realize **resonant circuits** by using **transmission lines** as reactive elements. For instance, consider the circuit below realized with lines having the same characteristic impedance:



$$Z_{in1} = j Z_0 \tan(\beta L_1)$$

$$Z_{in2} = j Z_0 \tan(\beta L_2)$$

The circuit is **resonant** if  $L_1$  and  $L_2$  are chosen such that an inductance and a capacitance are realized.

A **resonance condition** is established when the total input impedance of the parallel circuit is **infinite** (or, equivalently, when the input admittance of the parallel circuit is zero)

$$\frac{1}{j Z_0 \tan(\beta_r L_1)} + \frac{1}{j Z_0 \tan(\beta_r L_2)} = 0$$

or

$$\tan\left(\frac{\omega_r}{v_p} L_1\right) = -\tan\left(\frac{\omega_r}{v_p} L_2\right) \quad \text{with} \quad \beta_r = \frac{2\pi}{\lambda_r} = \frac{\omega_r}{v_p}$$

Since the tangent is a periodic function, there is a multiplicity of possible **resonant angular frequencies**  $\omega_r$  that satisfy the condition above. The solutions can be found by using a **numerical** procedure.